

from
*Assembly Language and Computer Architecture
Using C and C++*

Constructing a Microprogrammed Computer


Copyright © 2019 Anthony J. Dos Reis

Basic Electronics and Digital Logic

Digital Circuits

- *Combinational*: a circuit whose output depends only on its present inputs
- *Sequential*: a circuit whose output depends on its past as well as present inputs. That is, it depends on the *sequence* of inputs from the past up to the present.

 Atom has a positively-charged nucleus and negatively-charged orbiting electrons




Like charges repel.
Unlike charges attract

A conductor has electrons that are not “stuck” to the nucleus.

An insulator has no “unstuck” electrons.

A flashlight is a simple
electrical circuit


FIGURE 5.1

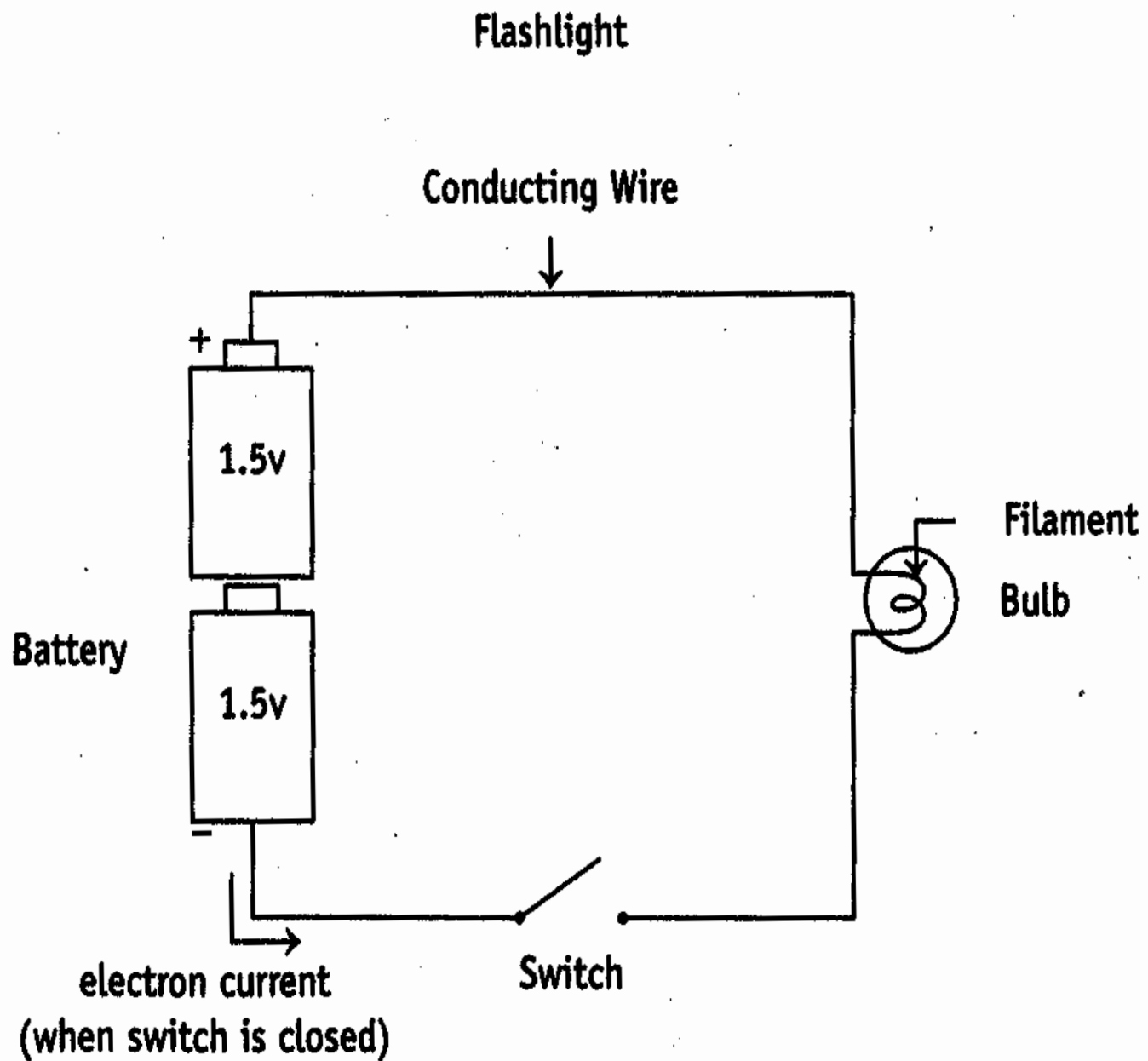

- Electron current – flow of electrons
- Voltage – provides “push” of electrons
- Resistance – opposition to current

FIGURE 5.2

Schematic Diagram

 

Ohm's law

I is current in amps

E is voltage in volts

R is resistance in ohms

$$I = E/R$$


Solving for E in Ohm's law

$$E = IR$$


Important observation:

The voltage across a resistor (the *voltage drop*) is zero if I (the current) is zero.

 Direct current (DC) flows in only one direction



 
Alternating current (AC) repeatedly changes its direction of flow.



Computers circuits cannot use the 117 volt *AC line voltage* available by household electrical outlets. A computer *power supply* converts line voltage to the DC voltage required by computer circuits.

FIGURE 5.3

Power Supplies

 


Safety rules with electricity

- Never touch any electrical equipment when any part of your body is wet.
- Never open electrical equipment unless you are qualified to do so.
- Keep one hand in your pocket while examining any electrical circuit.
- Never use any electrical equipment with frayed wires.

MOS transistors

- Low power consumption
- High noise immunity
- High fan out
- Three leads: source, drain, gate
- Two types: PMOS (P-type), NMOS (N-type)
- CMOS technology: PMOS, NMOS used in pairs to minimize current requirements


FIGURE 5.4

 


Inverter (NOT gate)

FIGURE 5.5


a)

 

b)

 

c)

 

Truth table for NOT

Input/output relationship:


in	out
0	3
3	1

If we let 0 and 3 volts represent the logic values 0 and 1, respectively, we get the truth table

in	out
0	1
1	0

FIGURE 5.6

a)

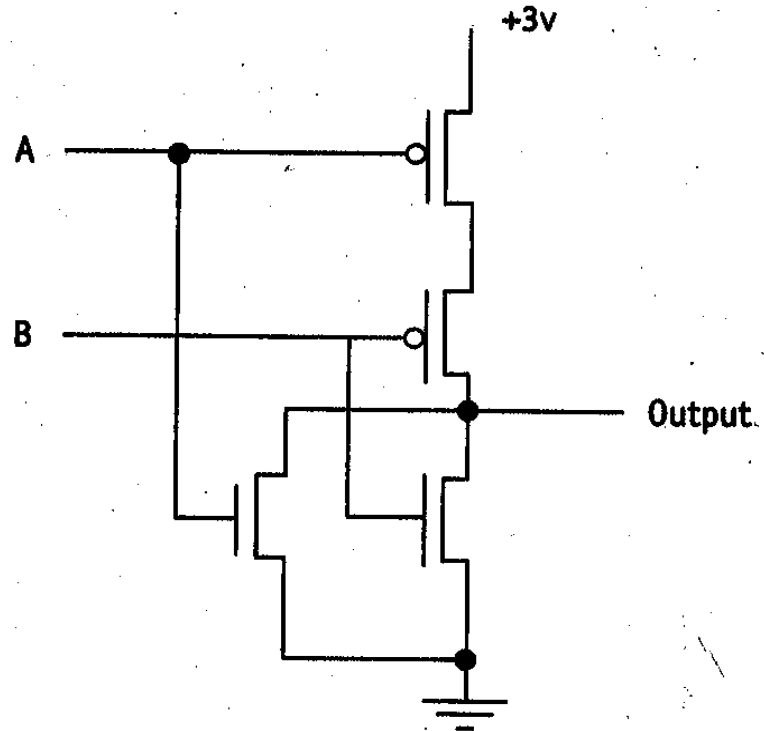NOR/NAND Function

b)

A	B	Output
0	0	3
0	3	0
3	0	0
3	3	0

c)

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

NOR

Positive logic


d)

A	B	Output
1	1	0
1	0	1
0	1	1
0	0	1

NAND


Negative logic



Tri-State Buffer

 

Input	Control	Output
0	0	High-Z
1	0	High-Z
0	1	0
1	1	1

Tri-State Buffer

 

  

Positive logic – the higher voltage value represents 1

Negative logic – the lower voltage value represents 1

A capacitor stores an electrical charge. When a capacitor is charging or discharging, current is flowing (and heat is generated).

FIGURE 5.7

Capacitance


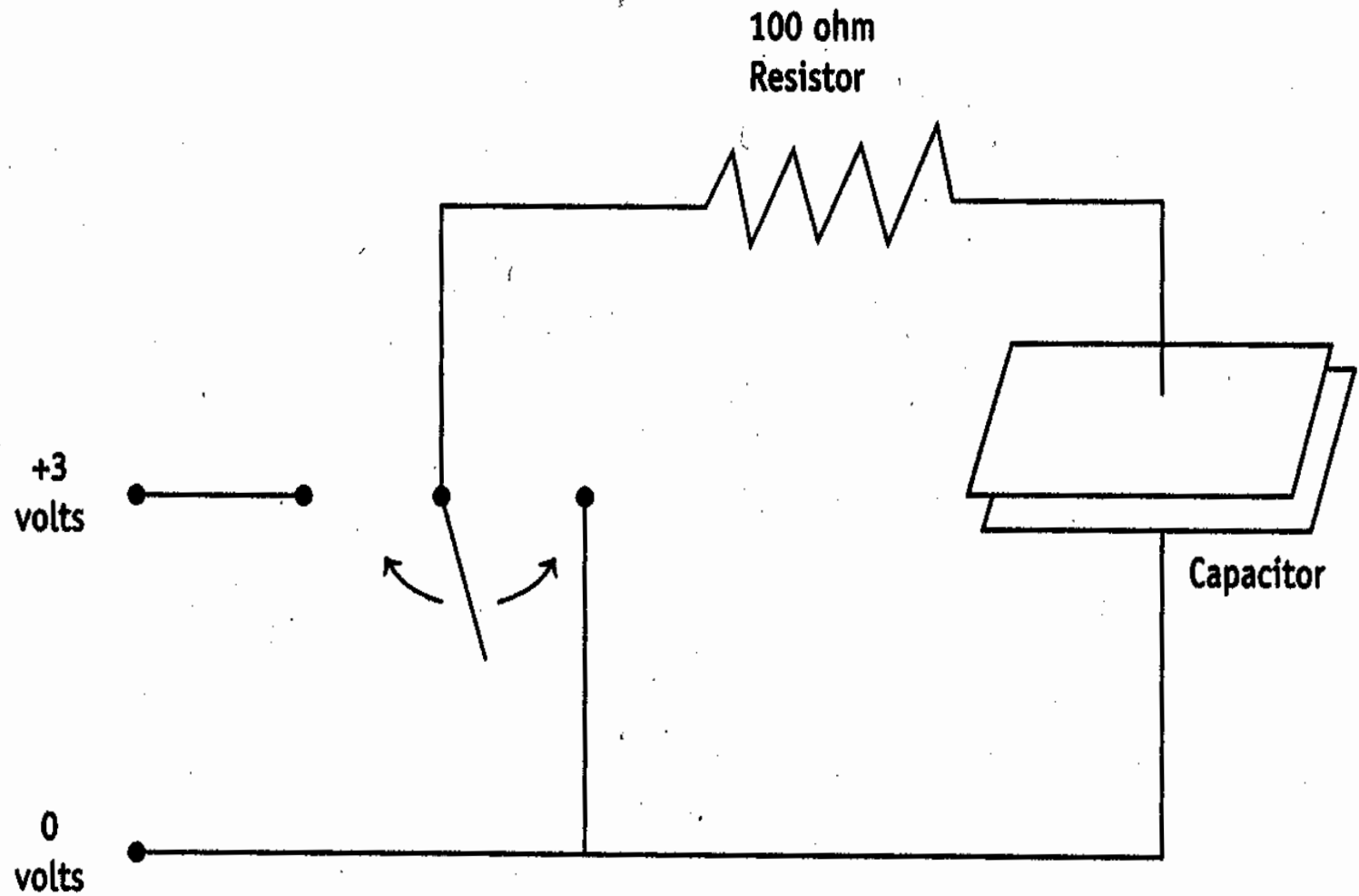


FIGURE 5.8

Resistor - Capacitor Circuit

 

The heat generated in our capacitor-resistor circuit is proportional to the frequency of voltage changes.

The heat generated is also proportional to the *square* of the magnitude of the voltage change.

To Make Computer Go Faster

- Increase clock speed
- Reduce size to decrease transit time from one subcircuit to another

Problem:

All circuits, including computer circuits, have capacitance.

Increasing clock frequency increases temperature.

Decreasing size increases temperature.

Computer circuits can be damaged by excessive temperature.

Solutions:


Reduce voltage to compensate for increasing frequency.

But must not make voltage differential too small.

Attach cooling devices.

Combinational Circuits

FIGURE 5.9

 

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

A	Output
0	1
1	0

Building AND and OR gates

FIGURE 5.10



 


FIGURE 5.11

Gating Action

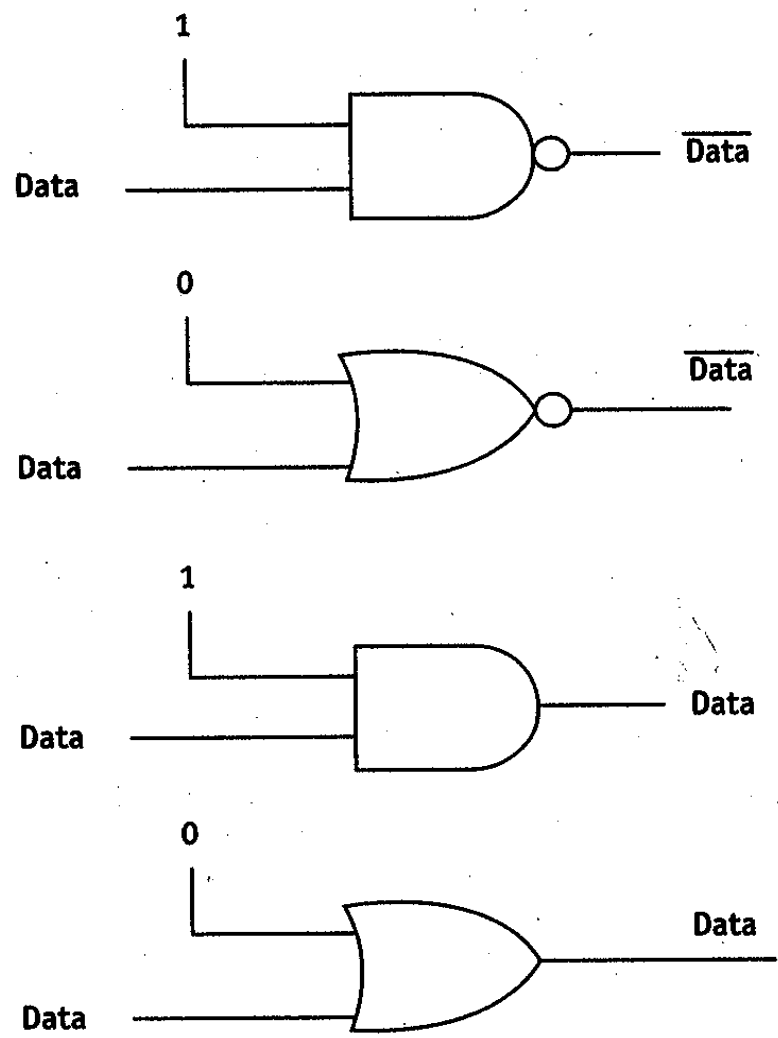

Gate "open"
(data passes through)

 

Gate "closed"
(data blocked)

It is easy to construct the circuit corresponding to any truth table.

Implementing circuit from truth table

FIGURE 5.12


A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

← select this row
← select this row

Build a circuit for each row with a 1 output, and then connect using an OR gate.

FIGURE 5.13

Implementing a Function

 

Note the resulting circuit contains
AND gates driving an OR gate.



There is more than one way to implement a truth table. The circuit with the least number of gates is called the *minimal* circuit.

FIGURE 5.14

Minimization

a)

A	B	C
0	0	1
0	1	1
1	0	0
1	1	0

  

Circuits can be minimized using any of several techniques. We will study two such techniques: Boolean algebra and Karnaugh maps.

Boolean expressions

- Describe operation of computer circuits
- '+' represents OR
- Concatenation represents AND
- Superscript bar represents NOT
- Two values: 1 and 0

$$C = \overline{A} \overline{B} + \overline{A} B$$

Describes of circuit on the next slide.

You can use Boolean algebra to simplify this expression (hint: factor out “A bar”).

$$C = \overline{A} \overline{B} + \overline{A} B$$

Using these laws, we can manipulate Boolean expressions into equivalent simpler expressions. For example, let's use Boolean algebra to simplify

$$C = \bar{A} \bar{B} + \bar{A} B$$

We get

$$\begin{aligned} C &= \bar{A} \bar{B} + \bar{A} B \\ &= \bar{A}(\bar{B} + B) \quad \text{by the distributive law} \\ &= \bar{A}(1) \quad \text{by the inverse law} \\ &= \bar{A} \quad \text{by the identity law} \end{aligned}$$

The laws of Boolean algebra are not identical to the laws of real number algebra.

FIGURE 5.15**Distributive Law**

$$A(B + C) = AB + AC$$

Commutative Law

$$A + BC = (A + B)(A + C)$$

Absorption Law

$$AB = BA$$

$$A + B = B + A$$

$$A + AB = A$$

Identity Law

$$A(A + B) = A$$

$$A1 = A$$

$$A + 0 = A$$

Null Law

$$A0 = 0$$

$$A + 1 = 1$$

Idempotent Law

$$A + A = A$$

$$AA = A$$

Inverse Law

$$A\bar{A} = 0$$

$$A + \bar{A} = 1$$

Associative Law

$$(A + B) + C = A + (B + C)$$

$$(AB)C = A(BC)$$

DeMorgan's Laws

$$\overline{A + B} = \bar{A}\bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

Bye, bye black sheep rule:

If two terms differ in only one variable, may combine terms by eliminating “black sheep” variable.

$$ABCD + AB\bar{C}D$$

Black sheep rules yields single term **ABD**

DeMorgan's Laws


$$\overline{A + B} = \overline{A} \overline{B}$$

$$\overline{AB} = \overline{A} + \overline{B}$$


FIGURE 5.16

De Morgan's Laws

a)

 


b)

 

Move bubble back: gate changes

In a circuit consisting of AND gates driving a single OR gate, all AND and OR gates can be replaced by NAND gates. The resulting circuit will realize the same function.

 FIGURE 5.17**NAND Gate Substitution**

Karnaugh map

- Matrix representation of a Boolean function
- Useful for circuit minimization
- Horizontally and vertically adjacent squares differ in only one variable. Thus, horizontal and vertical groups correspond to terms simplified by the black sheep rule.

FIGURE 5.18

a)

B \ A	0	1
0		1
1		1

This square corresponds to $A\bar{B}$

This square corresponds to AB

b)

A	B	C
0	0	0
0	1	0
1	0	1
1	1	1

$$C = A\bar{B} + AB$$

Black sheep rule yields

$$C = A$$

When the function below is simplified,
you have to use AB twice.

$$C = A\bar{B} + AB + \bar{A}B$$

$$= A\bar{B} + AB + AB + \bar{A}B$$

$$= (A\bar{B} + AB) + (AB + \bar{A}B)$$

$$= A + (AB + \bar{A}B)$$

$$= A + B$$

by the idempotent law

by the associative law

by the black sheep rule

by the black sheep rule

Now simplify same function using Karnaugh map. Note: using bottom right term (AB) twice

FIGURE 5.19

 


FIGURE 5.20

		AB			
		00	01	11	10
CD	00				
	01				
	11			1	1
	10			1	1

← This square corresponds to ABCD

Group corresponds to AC


FIGURE 5.21

		AB			
		00	01	11	10
CD	00	1			1
	01	1			1
	11	1			1
	10	1			1

Group corresponds to \overline{B}

Sequential Circuits

SR Latch

 


S	R	Q	Q'
0	1	0	1
0	0	0	1
1	0	1	0
0	0	1	0
1	1	0	0



Two rows for $S = R = 0$


Decoder


Two-bit decoder

 

Multiplexer

Four-input multiplexer

 

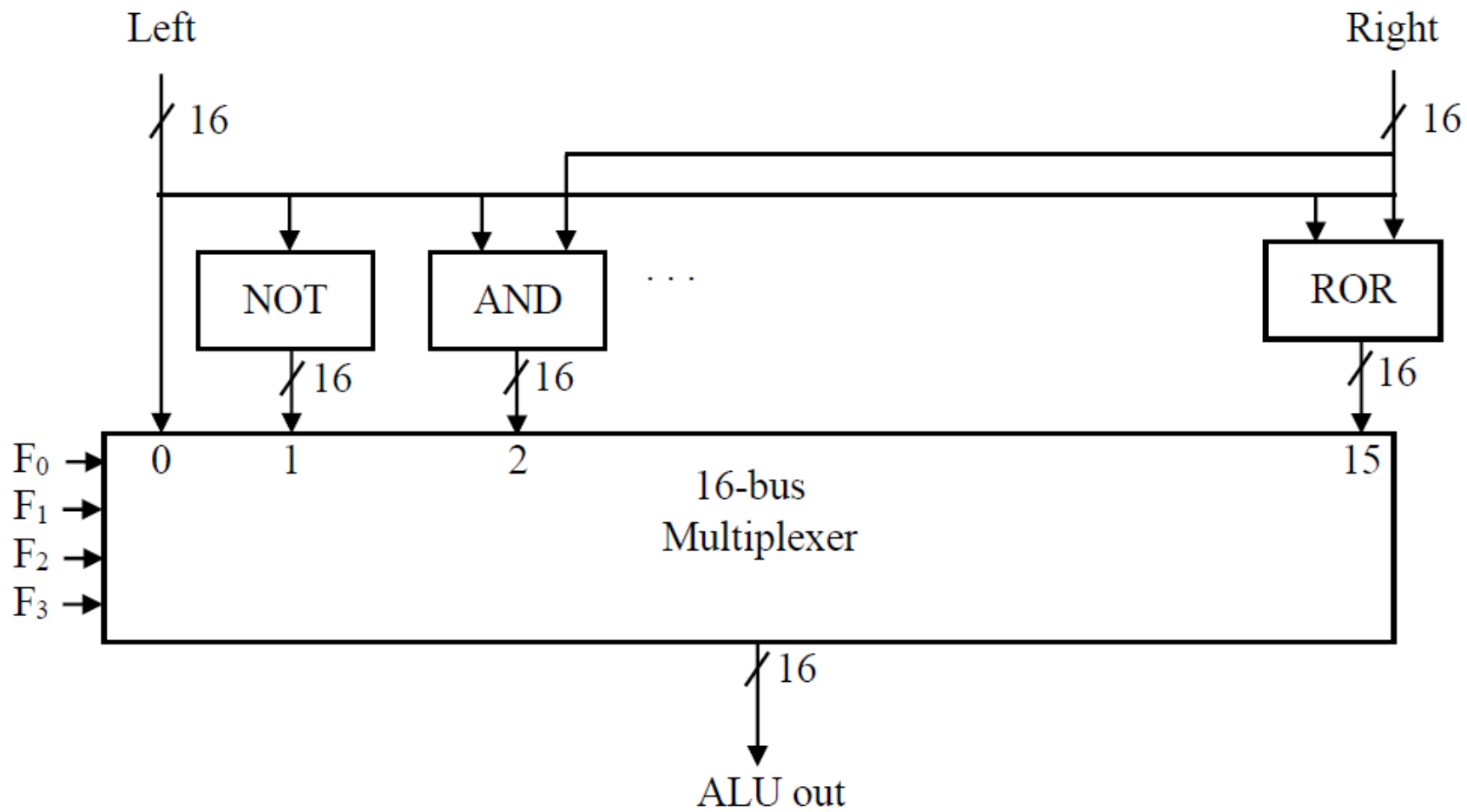

Random-Access and Read-Only Memory

